

Close the switch. Measure and record the current  $I_0$ .

$I_0 = \dots\dots\dots$  mA

(1 mark)

Dismantle the set up.

- ii) Set up the apparatus as shown in the circuit diagram in figure 3.

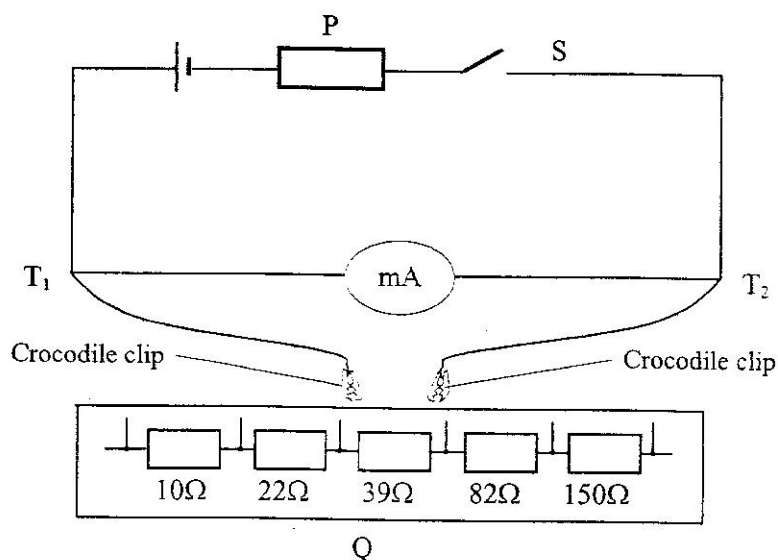


Figure 3

**Each of the connecting wires from points  $T_1$  and  $T_2$  should have a crocodile clip at one end.**

- iii) Connect the crocodile clips across the  $10\ \Omega$  resistor on **Q**. Close the switch and record in Table 2 the current  $I$  through the milliammeter. Open the switch.
- iv) Repeat the procedure in (c) for the other values of resistance  $R$  shown in table 2 (some values of  $R$  may be obtained by combining suitable resistors on **Q**). Complete the table.

Table 2

$R\ (\Omega)$	10	22	32	39	61	71	82	121	150
$I\ (\text{mA})$									
$I\ (\text{A})$									

(7 marks)